

Measurement Circuits and Modeling Techniques for Titanium Capacitors

Michael L. DeLibero

Case Western Reserve University

July 2015

Acknowledgements

- Dr. Merat
- Dr. Welsch
- Steven Ehret
- Thesis Committee
- Case Western Reserve University
- ARPA-E (contract DE-AR000016)

Outline

Background

Outline

Background

Purpose

Outline

Background

Purpose

Instrumentation

Outline

Background

Purpose

Instrumentation

Regression

Outline

Background

Purpose

Instrumentation

Regression

Modeling

Outline

Background

Purpose

Instrumentation

Regression

Modeling

Conclusion

Outline

Background

Purpose

Instrumentation

Regression

Modeling

Conclusion

Future Work

Background

- 2011 ARPA-E grant to Dr. Welsch.
- Titanium capacitors to replace tantalum.
- Availability, cost, energy and power density.

Purpose

- Design instrumentation for Ti capacitors.
- Characterize capacitor parameters.





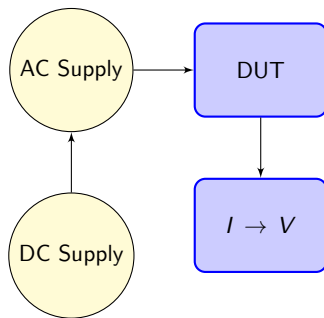



Figure: Circuit Flow Chart



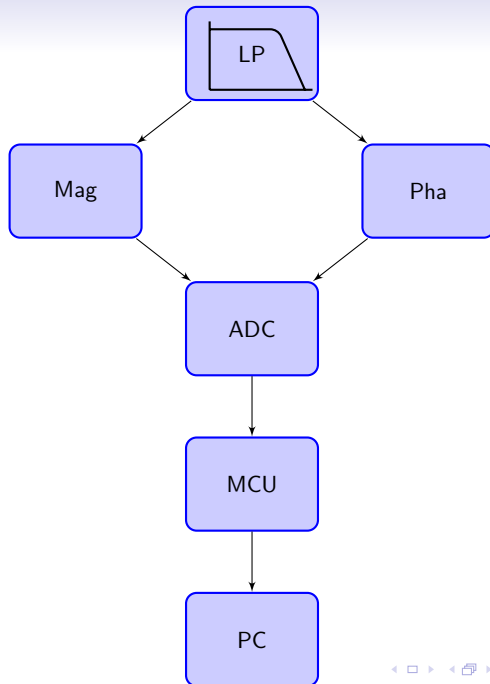


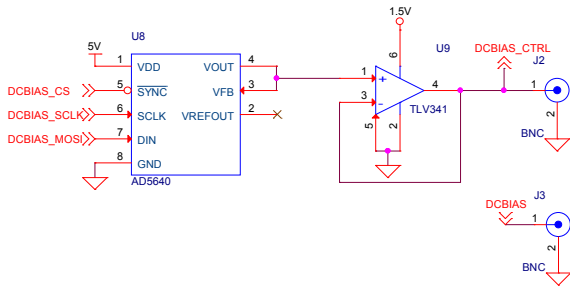


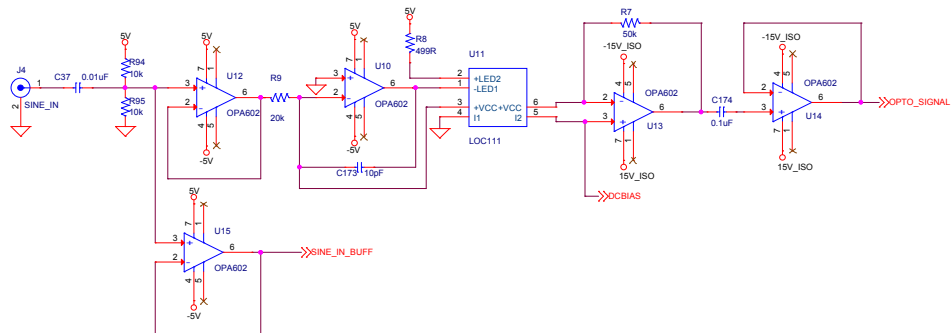

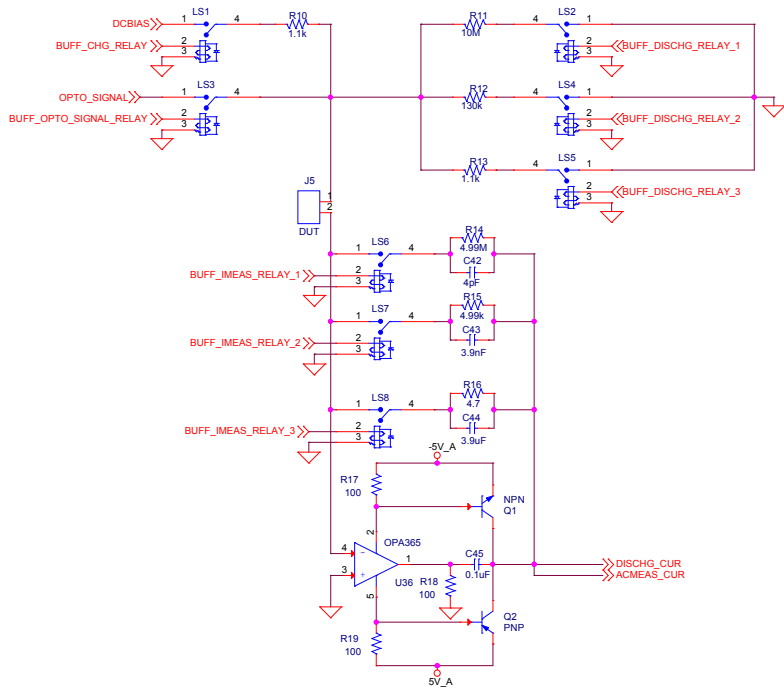


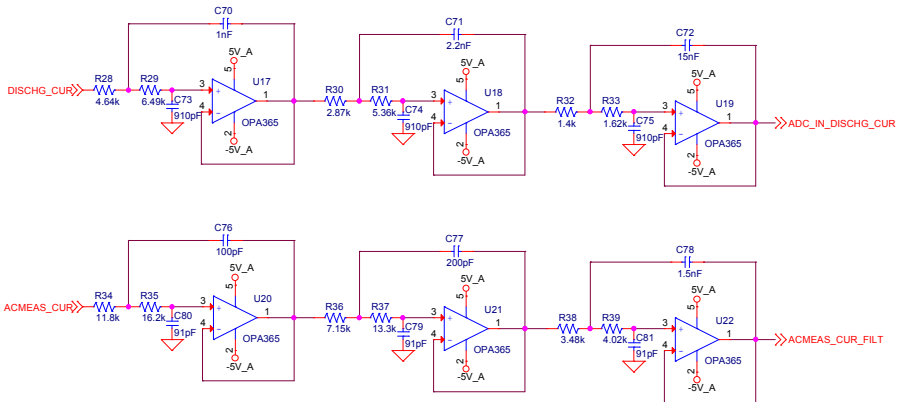

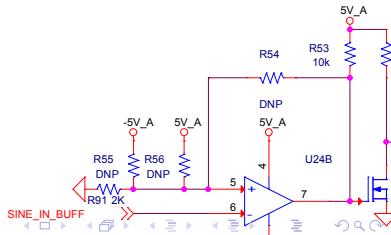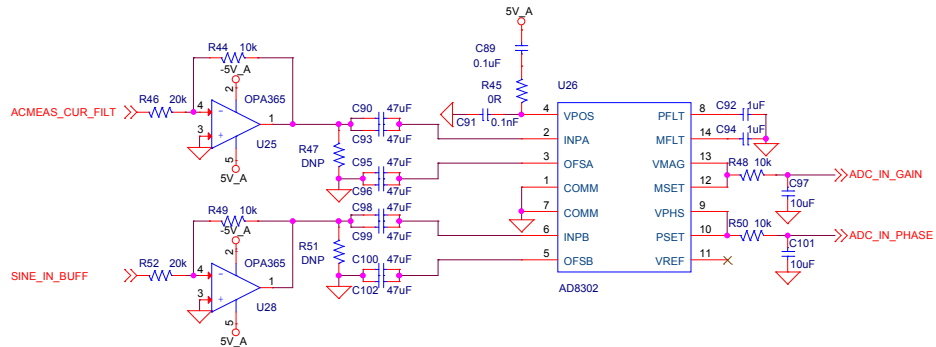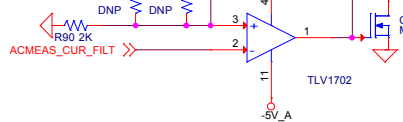

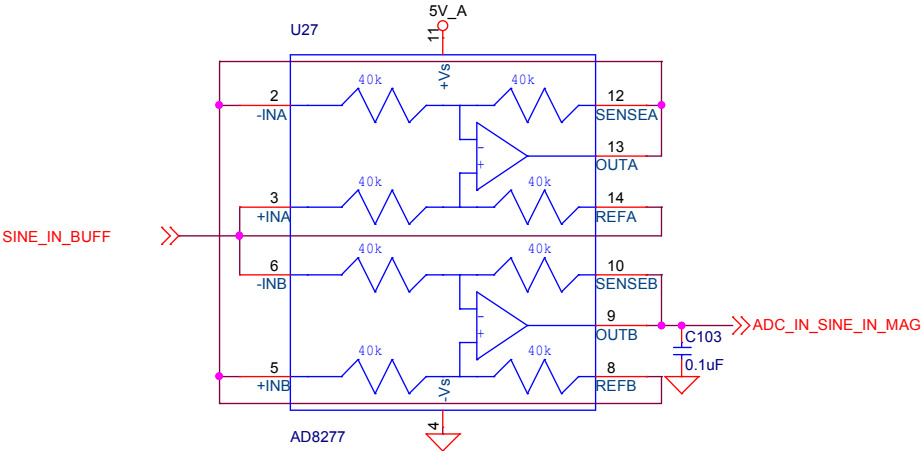

MAGNITUDE

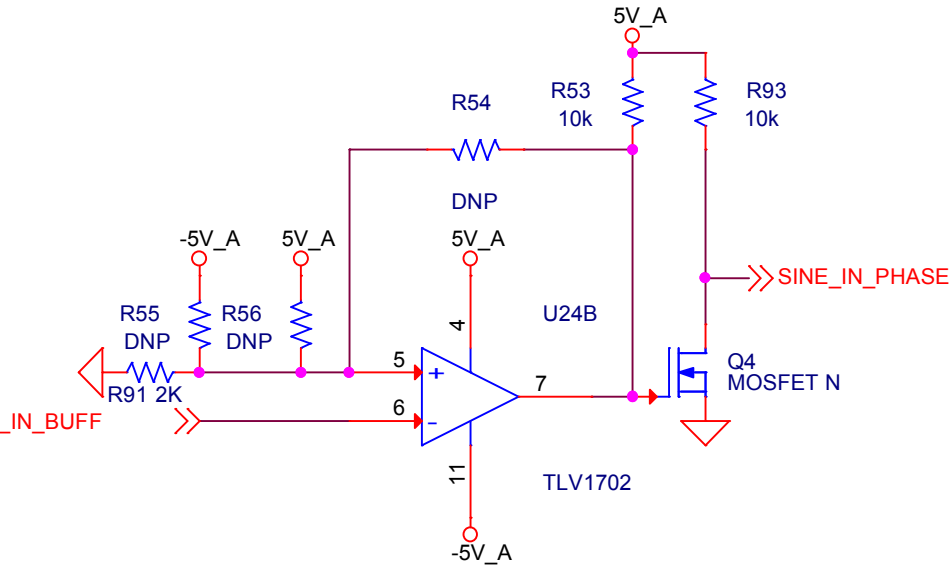

PHASE

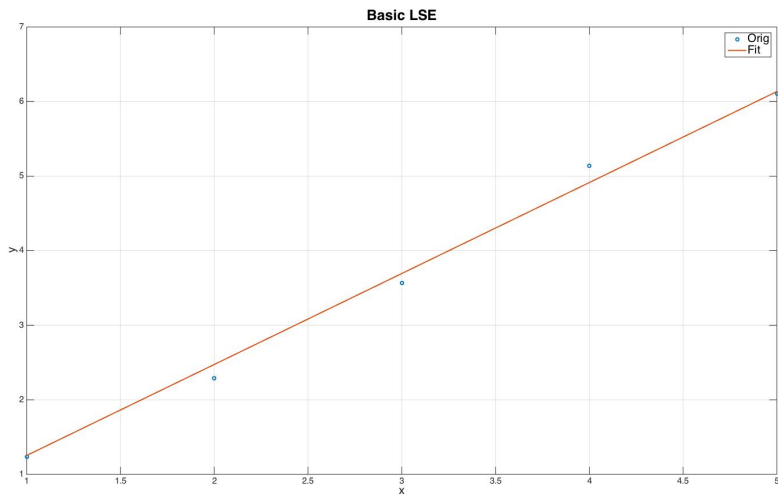


Figure: Basic LSE

Basic Regression

$$y = a_0 + a_1x \quad (1)$$

$$E^2 = \sum_{i=1}^n (y_i - y)^2 \quad (2)$$

$$E^2 = \sum_{i=1}^n (y_i - (a_0 + a_1x_i))^2 \quad (3)$$

$$\frac{\partial E^2}{\partial a_0} = 0 = \sum_{i=1}^n (-2y_i + 2a_0 + 2a_1x_i) \quad (4)$$

$$\frac{\partial E^2}{\partial a_1} = 0 = \sum_{i=1}^n (-2y_ix_i + 2a_0x_i + 2a_1x_i^2) \quad (5)$$

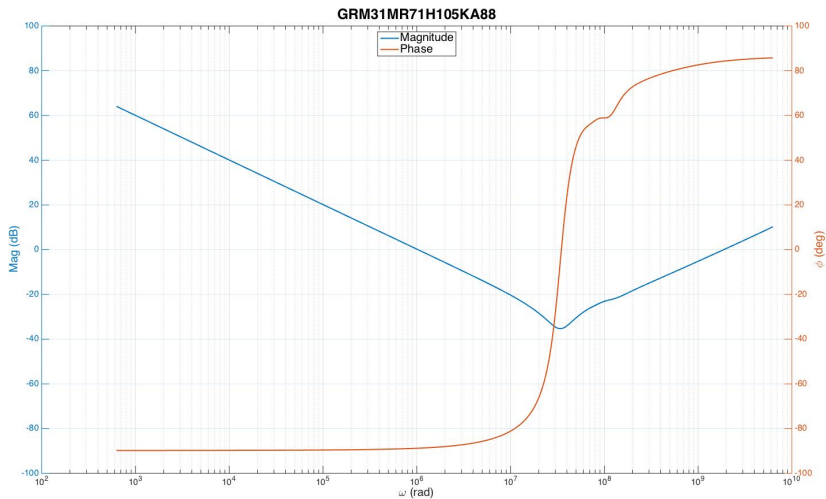


Figure: GRM31MR71H105KA88 Capacitor Data [3]

$$G(s) = \frac{A_0 + A_1s + A_2s^2 + \dots + A_ns^n}{B_0 + B_1s + B_2s^2 + \dots + B_ms^m} [1][Eq. 3] \quad (6)$$

$$\lambda_h = \sum_{k=0}^m \omega_k^h [1][Eq. 15] \quad (7)$$

$$S_h = \sum_{k=0}^m \omega_k^h R_k [1][Eq. 16] \quad (8)$$

$$T_h = \sum_{k=0}^m \omega_k^h I_k [1][Eq. 17] \quad (9)$$

$$U_h = \sum_{k=0}^m \omega_k^h (R_k^2 + I_k^2) [1][Eq. 18] \quad (10)$$

$$M = \begin{bmatrix} \lambda_0 & 0 & -\lambda_2 & 0 & \cdots & T_1 & S_2 & -T_3 & -S_4 & \cdots \\ 0 & \lambda_2 & 0 & -\lambda_4 & \cdots & -S_2 & T_3 & S_4 & -T_5 & \cdots \\ \lambda_2 & 0 & -\lambda_4 & 0 & \cdots & T_3 & S_4 & -T_5 & -S_6 & \cdots \\ 0 & \lambda_4 & 0 & -\lambda_6 & \cdots & -S_4 & T_5 & S_6 & -T_7 & \cdots \\ \vdots & \vdots & \vdots & \vdots & & \vdots & \vdots & \vdots & \vdots & \\ T_1 & -S_2 & -T_3 & S_4 & \cdots & U_2 & 0 & -U_4 & 0 & \cdots \\ S_2 & T_3 & -S_4 & -T_5 & \cdots & 0 & U_4 & 0 & -U_6 & \cdots \\ T_3 & -S_4 & -T_5 & S_6 & \cdots & U_4 & 0 & -U_6 & 0 & \cdots \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \end{bmatrix} \quad [1][Eq. 21a]$$

(11)

$$N = \begin{bmatrix} A_0 \\ A_1 \\ A_2 \\ A_3 \\ \vdots \\ B_1 \\ B_2 \\ B_3 \\ \vdots \end{bmatrix} \quad [1][Eq. 21b] \quad (12) \quad C = \begin{bmatrix} S_0 \\ T_1 \\ S_2 \\ T_3 \\ \vdots \\ 0 \\ U_2 \\ 0 \\ \vdots \end{bmatrix} \quad [1][Eq. 21c] \quad (13)$$

$$MN = C \quad [1][Eq. 20] \quad (14)$$

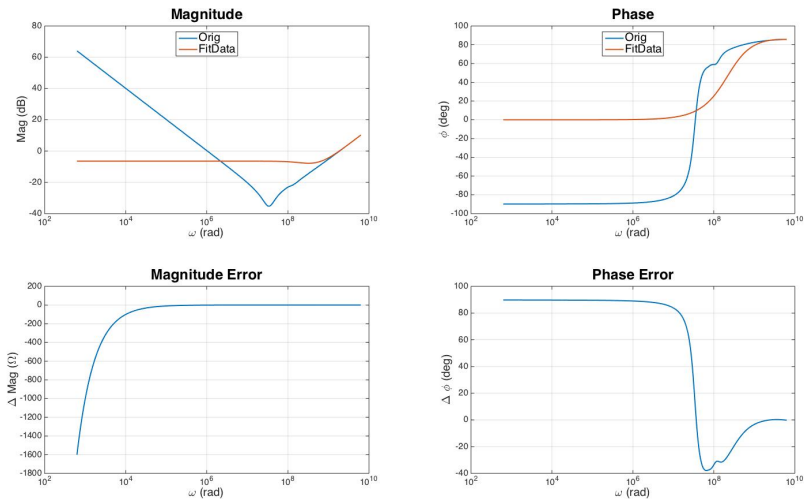


Figure: Levy's Technique

$$W_{kL} = \frac{1}{|Q(jw_k)_{L-1}|^2} [2] \quad (15)$$

$$E = \sum_{k=1}^n |\epsilon'_k|^2 W_{kL} [2][Eq. 7] \quad (16)$$

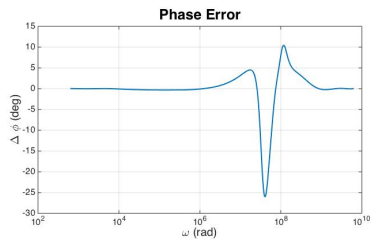
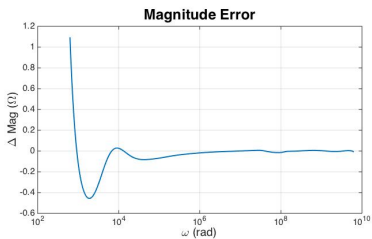
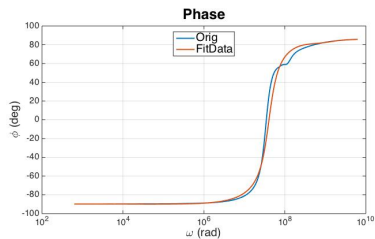
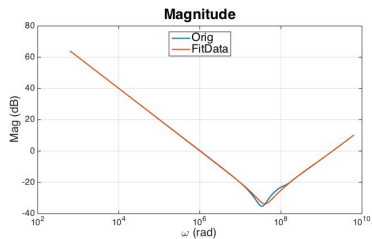


Figure: LSE + Iteration

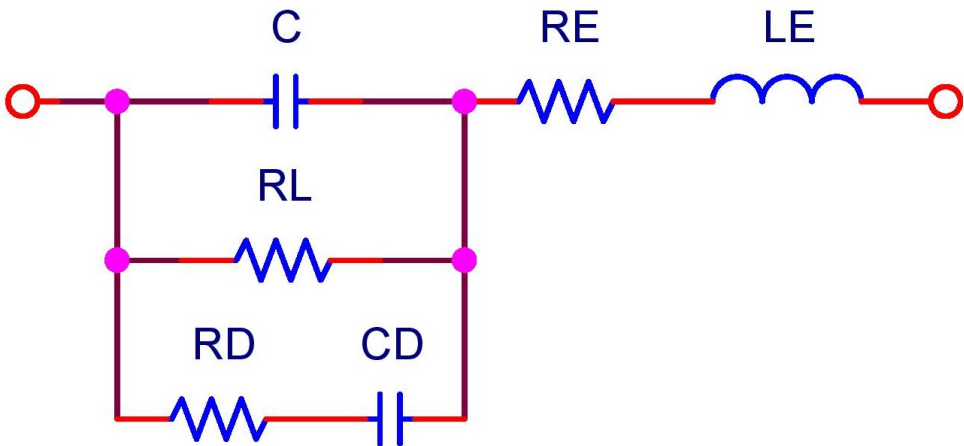


Figure: 6 Term Model

$$\bar{Z}(s) = \frac{(R_E + R_L) + (L_E + C_D R_D R_E + C_D R_D R_L + C R_E R_L + C_D R_E R_L)s}{1 + (C_D R_D + C R_L + C_D R_L)s + C C_D R_D R_L s^2} + \frac{(C_D L_E R_D + C L_E R_L + C_D L_E R_L + C C_D R_D R_E R_L)s^2 + C C_D L_E R_D R_L s^3}{1 + (C_D R_D + C R_L + C_D R_L)s + C C_D R_D R_L s^2} \quad (17)$$

$$\bar{Z}(s) = \frac{a_0 + a_1 s + a_2 s^2 + a_3 s^3}{b_0 + b_1 s + b_2 s^2} \quad (18)$$

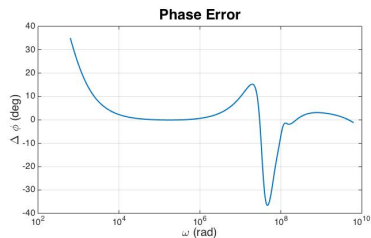
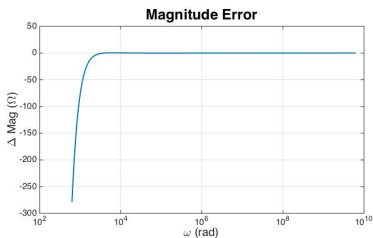
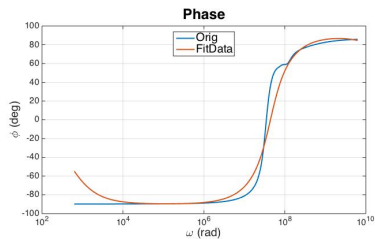
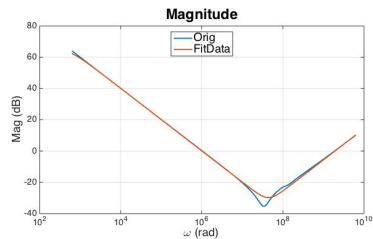


Figure: 6 Term Model: Bad Initilization

$$\begin{aligned}a_0 &= 5.9991E^{+03} \\a_1 &= 1.7934E^{-04} \\a_2 &= 3.3158E^{-12} \\a_3 &= 6.8295E^{-22} \\b_0 &= 1.0000 \\b_1 &= 5.9057E^{-03} \\b_2 &= 1.4067E^{-12}\end{aligned}\quad (19)$$

$$\begin{aligned}C &= -8.2563E^{-10} \\R_E &= 3.1886E^{-01} \\L_E &= 4.8551E^{-10} \\R_L &= 4.8551E^{-10} \\C_D &= 9.8536E^{-07} \\R_D &= -2.8824E^{-01}\end{aligned}\quad (20)$$

$$\begin{aligned}a_0 &= 1 \\a_1 &= 1 \\a_2 &= 1 \\a_3 &= 1 \\b_0 &= 1 \\b_1 &= 0 \\b_2 &= 0\end{aligned}\tag{21}$$

$$\begin{aligned}C &= INF \\R_E &= INF \\L_E &= INF \\R_L &= IND \\C_D &= IND \\R_D &= IND\end{aligned}\tag{22}$$

$$\begin{aligned}a_0 &= 2 \\a_1 &= 5 \\a_2 &= 4 \\a_3 &= 1 \\b_0 &= 1 \\b_1 &= 3 \\b_2 &= 1\end{aligned}\tag{23}$$

$$\begin{aligned}C &= 1 \\R_E &= 1 \\L_E &= 1 \\R_L &= 1 \\C_D &= 1 \\R_D &= 1\end{aligned}\tag{24}$$

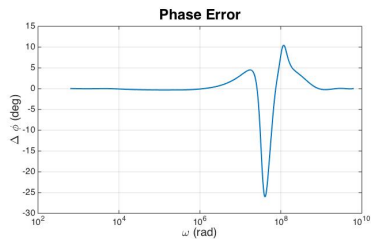
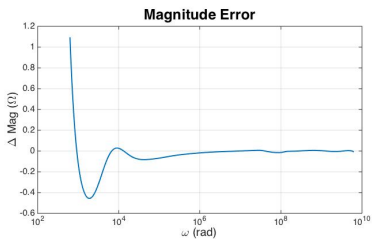
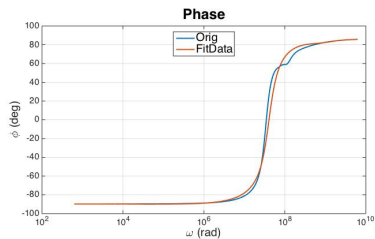
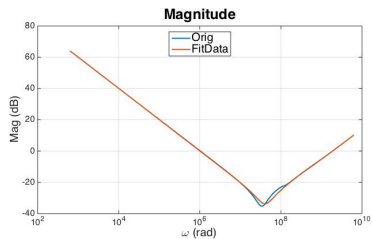


Figure: 6 Term Model: Good Initialization

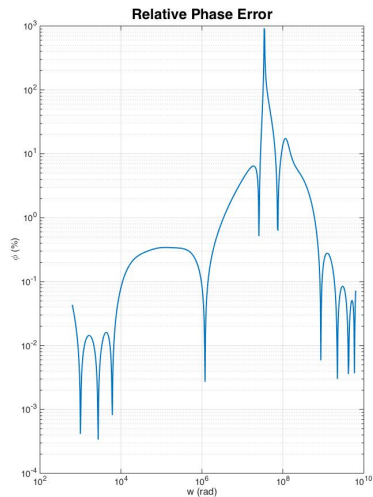
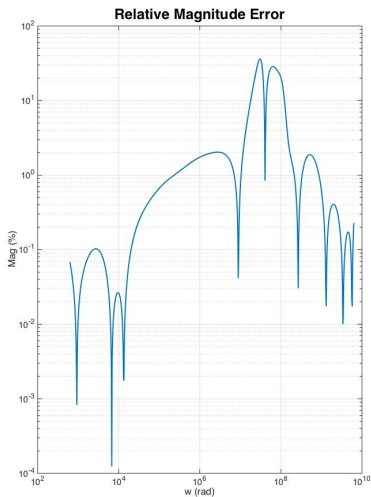


Figure: 6 Term Model: Relative Error

Conclusion

Circuit Capabilities:

- Discharge Curve
- Impedance

Measurement Range:

- DC bias range 0→500V.
- Frequency Range of 100Hz→40kHz.

Regression Accuracy:

- Accurate outside of resonance.
- 2Ω and 2° .
- $< 5\%$.

Future Work

- Build the circuit and validate against the stated capabilities and accuracy.
- Increase the available frequency range for the measurement circuitry.
- Add additional fail-safe protection to the circuit.
- Update the regression technique for better accuracy.
- Evaluate the accuracy of the six term model.



E. C. Levy.

Complex-curve fitting.

Automatic Control, IRE Transactions on, AC-4(1):37–44,
1959.



C. K. Sanathanan and J. Koerner.

Transfer function synthesis as a ratio of two complex
polynomials.

Automatic Control, IEEE Transactions on, 8(1):56–58, Jan
1963.



Sim surfing.

[http://ds.murata.co.jp/software/simsurfing/en-us/
index.html?intcid5=com_xxx_xxx_cm_nv_xxx](http://ds.murata.co.jp/software/simsurfing/en-us/index.html?intcid5=com_xxx_xxx_cm_nv_xxx).

Questions?